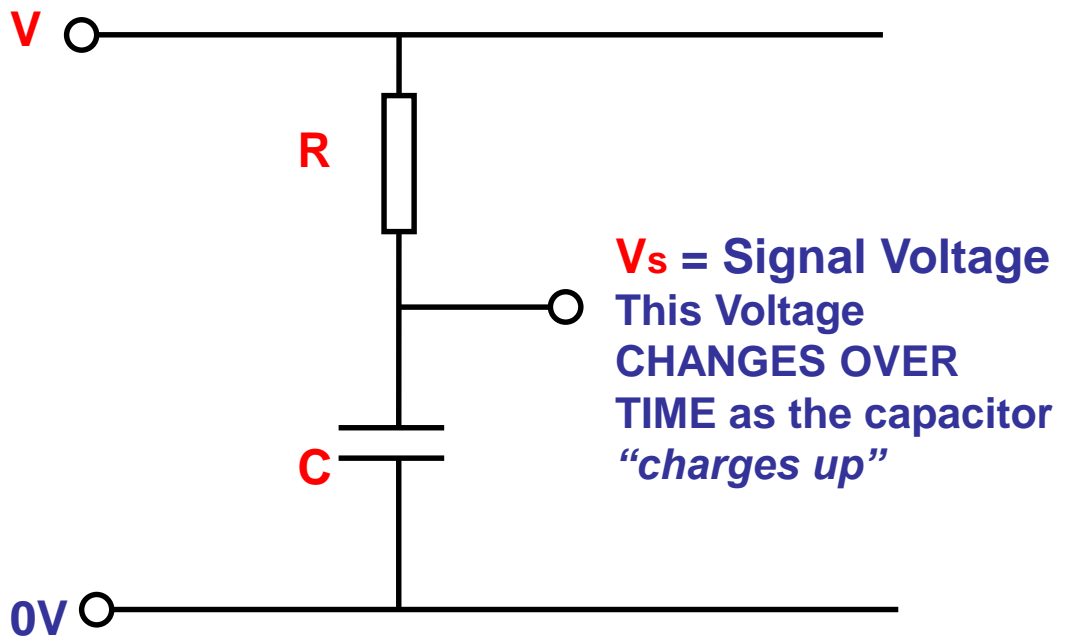


Timers

Potential Dividers with CAPACTITORS in them can be used for TIMING



The resistor slows down the current which then flows into the Capacitor. As the capacitor “fills up” (becomes fully charged) it’s resistance increases and V_s gets larger and larger.

Changing the Values of either the Resistor (R) or the Capacitor (C) will change the TIME CONSTANT (T)

The TIME CONSTANT is a fancy name for how long it takes a capacitor to charge up from current through a resistor.

The Time Constant can be calculated using this formula...

$$T = R \times C \text{ (roughly)}$$

TIME IS MEASURED IN SECONDS

But USE YOUR COMMON SENSE to check your answer!